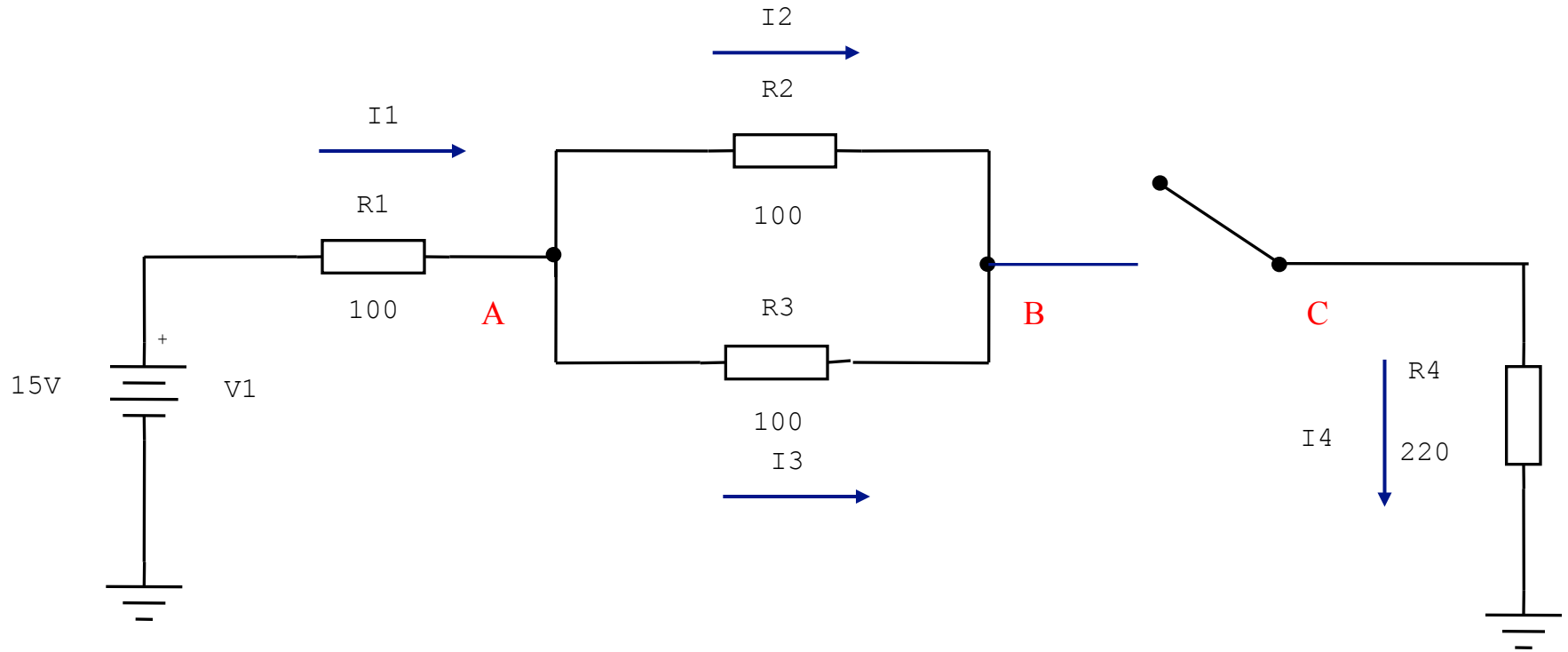





Review of circuit theory. Example 1



Open switch




Review of circuit theory. Example 1

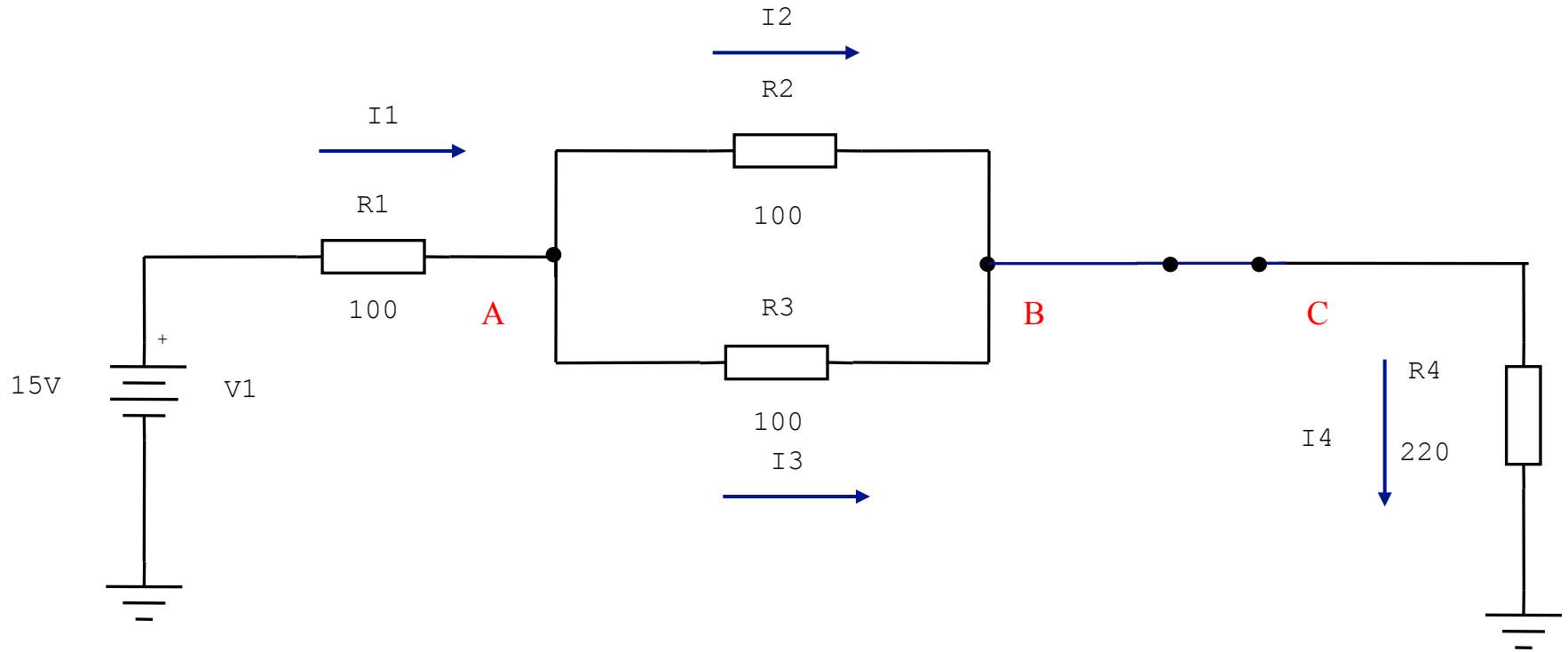

Closed switch



Review of circuit theory. Example 2

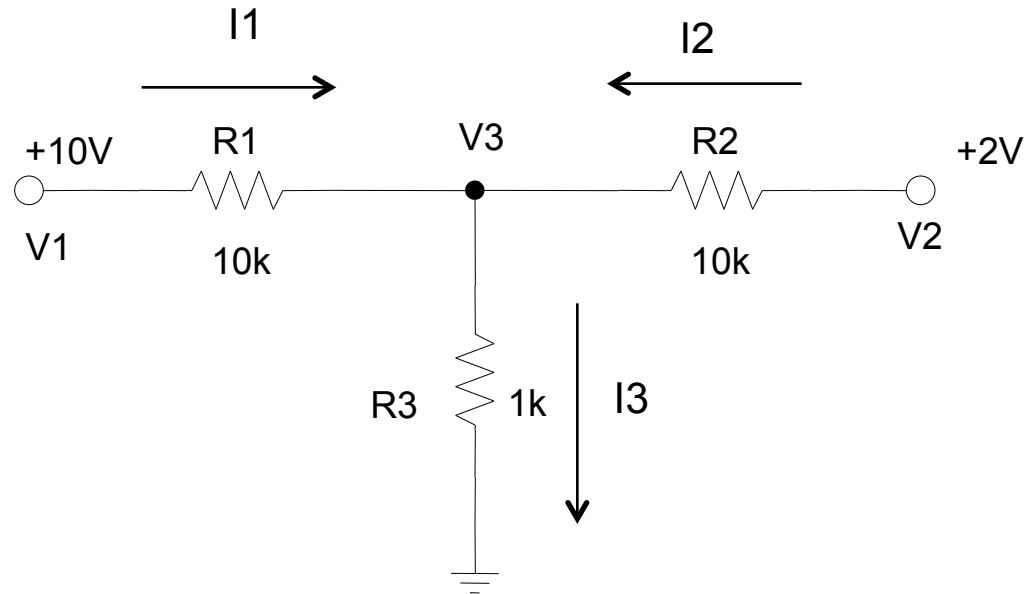

Solve the circuit, obtaining all voltages and currents